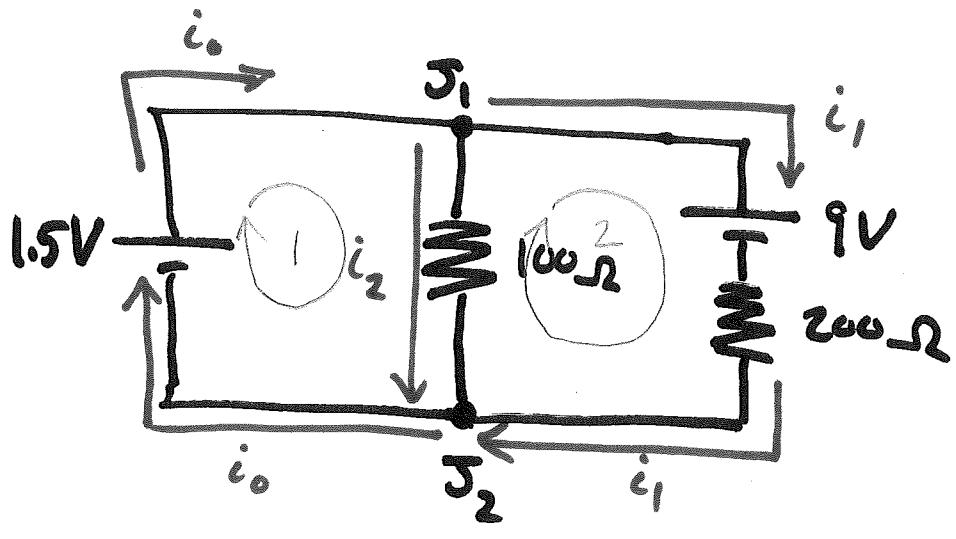


Ex 1



JR : $i_0 = i_1 + i_2$

LR : $-i_2(100\Omega) + 1.5V = 0$

$-9V - i_1(200\Omega) + i_2(100\Omega) = 0$

$i_2(100) = 1.5 \Rightarrow i_2 = 0.015 \text{ A}$

$-9 - i_1(200) + (0.015)(100) = 0$

$-i_1(200) = +7.5$

$i_1 = -0.0375 \text{ A}$

$i_0 = -0.0375 + 0.015 = -0.0225 \text{ A} = i_0$

$$V_{100\Omega} = (0.015A)(100\Omega) = \boxed{1.5V}$$

$$V_{200\Omega} = (0.0375)(200\Omega) = \boxed{7.5V}$$


$$P_{100\Omega} = (0.015A)(1.5V) = \boxed{0.0225W}$$

$$P_{200\Omega} = (0.0375)(\del{200} 7.5V) = \boxed{0.281W}$$

ex 2 - Have them do

prob 20.85

21

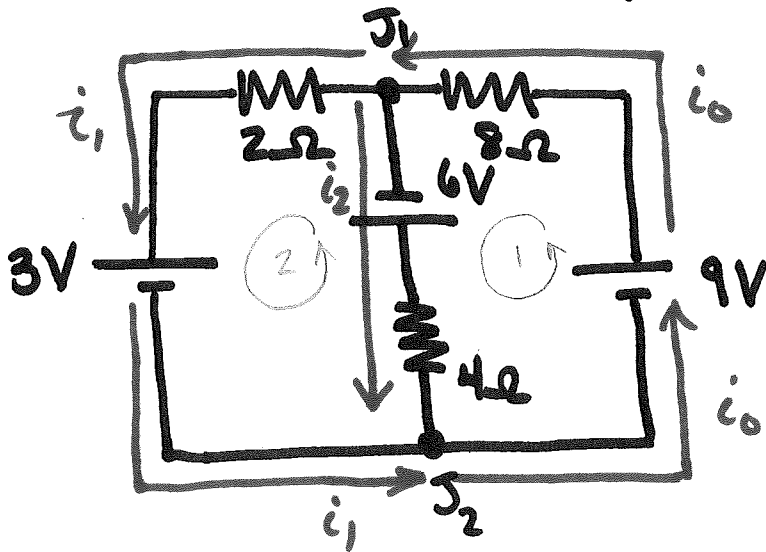

Find P dissipated across each resistor.

JR: $i_0 = i_1 + i_2$

LR: $-i_0(8\Omega) + 6V - i_2(4\Omega) + 9V = 0$

~~LR: $-i_1(2\Omega) - 3V + i_2(4\Omega) - 6V = 0$~~

~~$4i_2 = 9 + 2i_1 \Rightarrow i_2 = \frac{9}{4} + \frac{1}{2}i_1$~~

$-i_0 8 = -15 + 4i_2 \Rightarrow i_0 = \frac{15}{8} - \frac{1}{2}i_2$

$-2i_1 = 9 - 4i_2 \Rightarrow i_1 = -\frac{9}{2} + 2i_2$

$\frac{15}{8} - \frac{1}{2}i_2 = -\frac{9}{2} + 2i_2 + i_2$

$\frac{15}{8} + \frac{9}{2} = \frac{7}{2}i_2 \Rightarrow \boxed{i_2 = 1.82 \text{ A}}$

$$-i_0 8 + 15 - (1.82)4 = 0$$

$$i_0 = 0.965 \text{ A}$$

$$0.965 = i_1 + 1.82$$

$$i_1 = -0.855 \text{ A}$$

~~$$P_{2\Omega} = (0.855 \text{ A})$$~~

$$V_{2\Omega} = (0.855 \text{ A})(2\Omega) = 1.71 \text{ V}$$


$$V_{4\Omega} = (1.82 \text{ A})(4\Omega) = 7.28 \text{ V}$$

$$V_{8\Omega} = (0.965 \text{ A})(8\Omega) = 7.72 \text{ V}$$


$$P_{2\Omega} = (0.855 \text{ A})(1.71 \text{ V}) = 1.46 \text{ W}$$

$$P_{4\Omega} = (1.82 \text{ A})(7.28 \text{ V}) = 13.25 \text{ W}$$
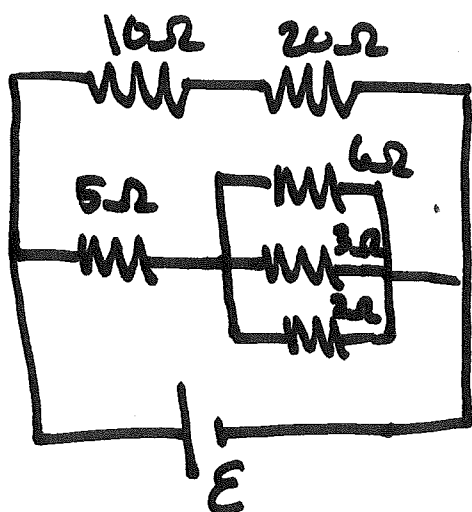
$$P_{8\Omega} = (0.965 \text{ A})(7.72 \text{ V}) = 7.45 \text{ W}$$





A) Determine the Equivalent Resistance

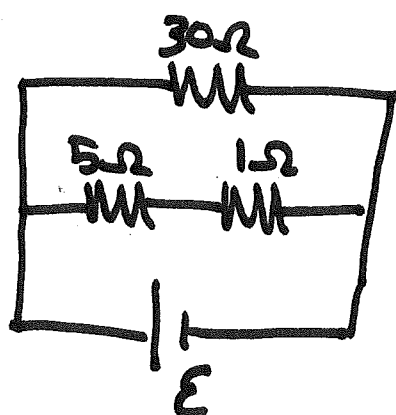

$$\frac{1}{R} = \frac{1}{6} + \frac{1}{3} + \frac{1}{2} = \frac{1}{6} + \frac{2}{6} + \frac{3}{6} = 1$$

$$R = 1\Omega$$

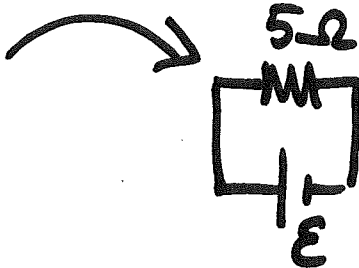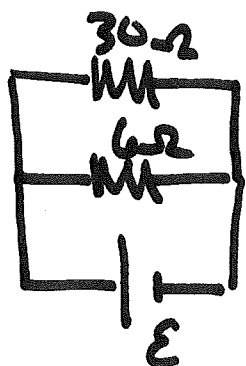


$$\frac{1}{R_{eq}} = \frac{1}{30} + \frac{1}{6} = \frac{6}{30}$$

$$R_{eq} = 5\Omega$$

$$R_{eq} = 5\Omega$$

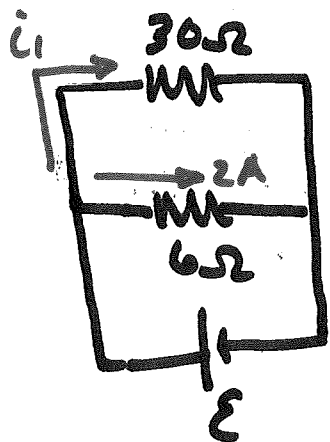B) If the current through the 5Ω resistor is $2A$, find all the other currents.



$$V_{6\Omega} = E = (2A)(6\Omega) = 12V$$

$$E = 12V$$

Find i_{battery}

$$E = i_0 R_{\text{eq}}$$

$$12V = i_0 (5\Omega)$$

$$i_0 = 2.4A$$

$$i_0 = i_1 + 2A$$

$$i_1 = 0.4A$$

$$i_{10\Omega} = i_{30\Omega} = 0.4A$$

$$V_{5\Omega} = (2A)(5\Omega) = 10V \Rightarrow V_{2\Omega} = V_{3\Omega} = V_{6\Omega} = 2V$$

$$i_{6\Omega} = \frac{2V}{6\Omega} \Rightarrow i_{6\Omega} = \frac{1}{3}A$$

$$i_{3\Omega} = \frac{2V}{3\Omega} \Rightarrow i_{3\Omega} = \frac{2}{3}A$$

$$i_{2\Omega} = \frac{2V}{2\Omega} \Rightarrow i_{2\Omega} = 1A$$

c) Find the total power dissipated by the resistors.

$$V_2 = V_3 = V_6 = 2V$$

$$V_{10} = (0.4A)(10\Omega) = 4V$$

$$V_5 = 10V$$

$$V_8 = 8V$$

$$P_2 = (1A)(2V) = \boxed{2W}$$

$$P_3 = \left(\frac{2}{3}A\right)(2V) = \boxed{\frac{4}{3}W}$$


$$P_6 = \left(\frac{1}{3}A\right)(2V) = \boxed{\frac{2}{3}W}$$

$$P_5 = (2A)(10V) = \boxed{20W}$$

$$P_{10} = (0.4A)(4V) = \boxed{1.6W}$$

$$P_8 = (0.4A)(8V) = \boxed{3.2W}$$

$$P_T = \sum P_i = \boxed{28.8W}$$

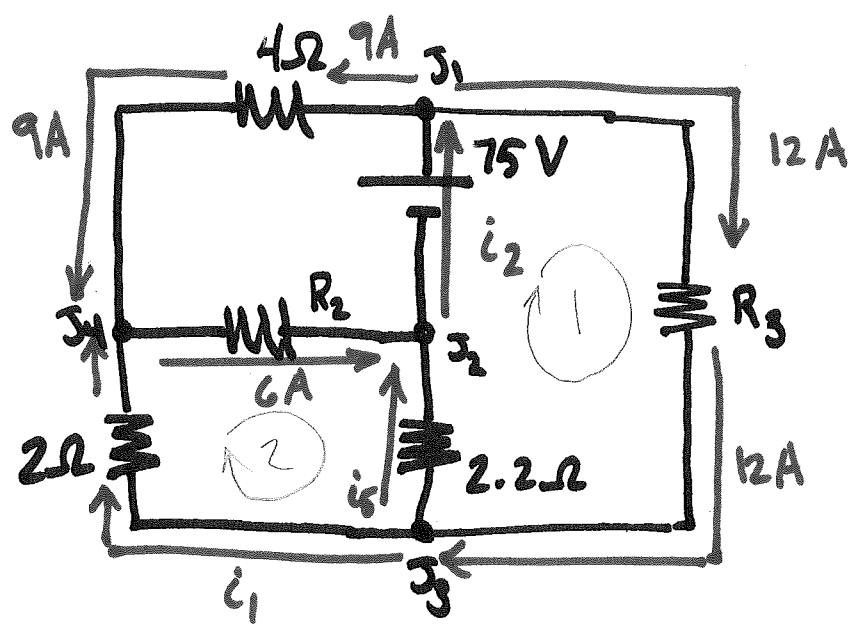

JR1 1: $i_2 = 9A + 12A = \boxed{21A}$

2: $6A + i_5 = i_2 = 21A$
 $\boxed{i_5 = 15A}$

3: $12A = i_1 + i_5 = i_1 + 15A$
 $\boxed{i_1 = -3A}$

4: Repeat $9 - 3 = \underline{6}$

LR1

$$1: -12R_3 - (15A)(2.2\Omega) + 75 = 0$$

$$-12R_3 = -42$$

$$R_3 = 3.5\Omega$$

$$2: -6R_2 + (15A)(2.2\Omega) - i_1(2\Omega) = 0$$

$$-6R_2 + 33 + 6 = 0$$

$$-6R_2 = -39$$

$$R_2 = 6.5\Omega$$